

Student Name: Alp Tuna

Student ID: 2019400288

CMPE 240 2021 Experiment 4 Preliminary Work

(For illustrations you can use any drawing tool that you want including Microsoft Word Shapes. Do not use scanned images of hand drawn state machines and architecture diagrams.)

(For tables please use insert table feature of Microsoft Word)

Step 1.1: State Register Inputs: n0, n1

Step 1.2: State Register Outputs: s0, s1

Step 2.1: Combinational Block Inputs: a, b, s0, s1

Step 2.2: Combinational Block Outputs: y0, y1, n0, n1

Step 3: Obtain the truth table:

$$y1 = a.s1' + a.b'.s0'$$

$$y0 = a'.b + s0.s1 + b.s1$$

$$n1 = a.s1' + a.b'.s0'$$


$$n0 = b.s0' + s0.s1 + b.s1$$

s1	s0	a	b	n1	n0	y1	y0
0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	1
0	0	1	0	1	0	1	0
0	0	1	1	1	1	1	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	0
1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	1
1	0	1	0	1	0	1	0
1	0	1	1	0	1	0	1
1	1	0	0	0	1	0	1
1	1	0	1	0	1	0	1
1	1	1	0	0	1	0	1
1	1	1	1	0	1	0	1

Student Name: Alp Tuna
Student ID: 2019400288

Step 4: Draw the finite state machine:

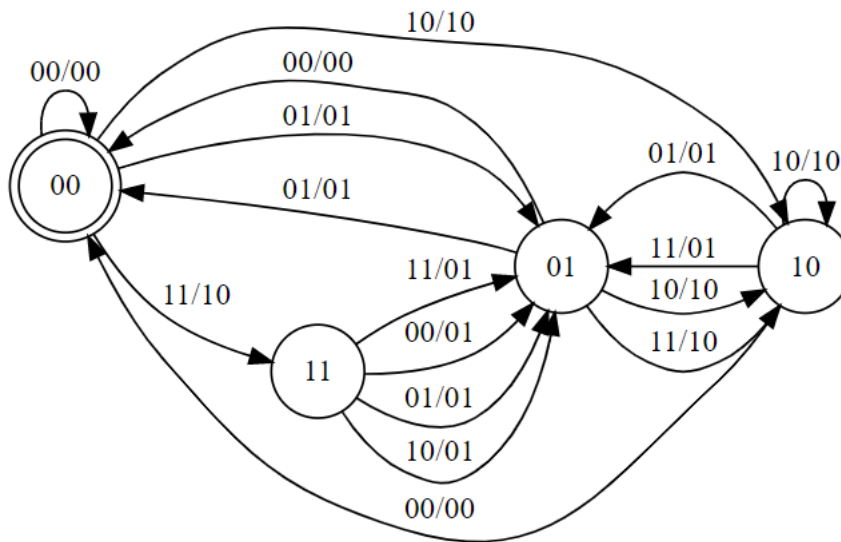Edge format is as follows $\rightarrow ab / y_1y_0$



Step 5: Is this a Moore or Mealy Machine? (No explanations, only short answer):
MEALY